

Computing in carbon

Neuroelectronics


- membranes
- ion channels
- wiring

Simplified neuron models




- the basic dynamics of neuronal excitability

Neuronal geometry


- Dendrites and dendritic computing

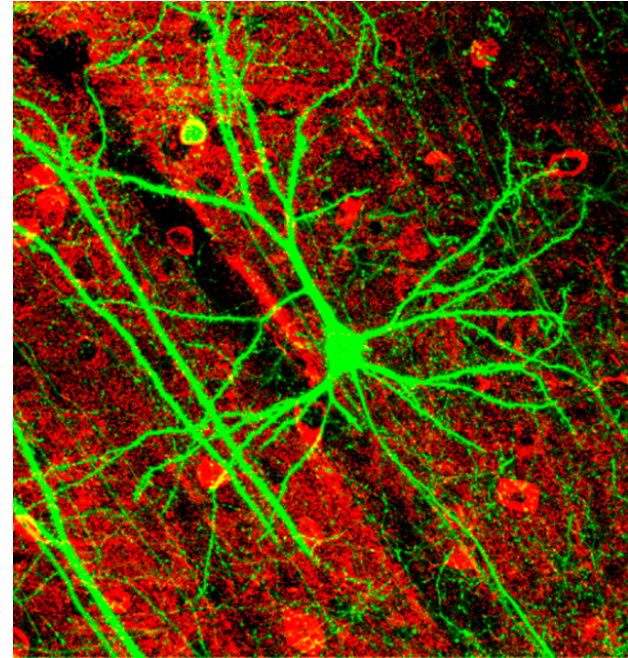

Equivalent circuit model

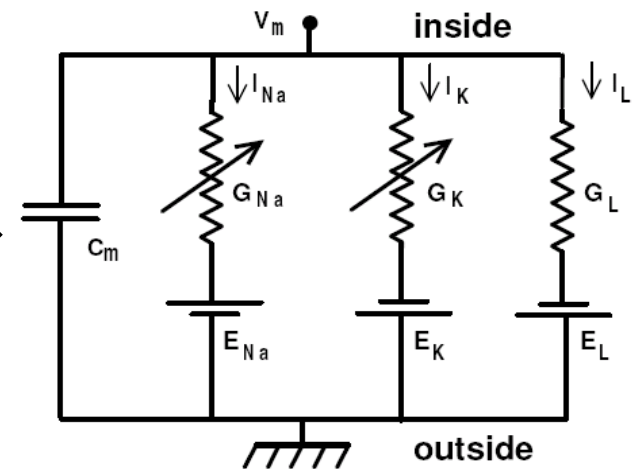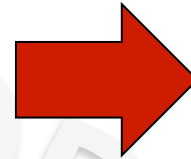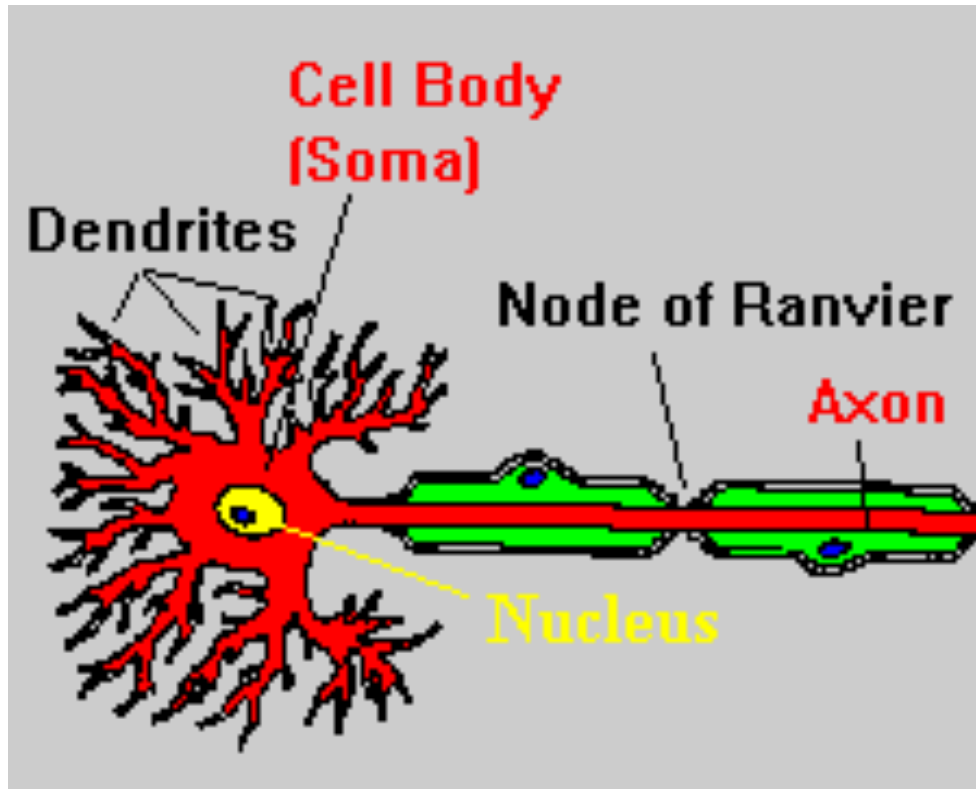


RC circuits


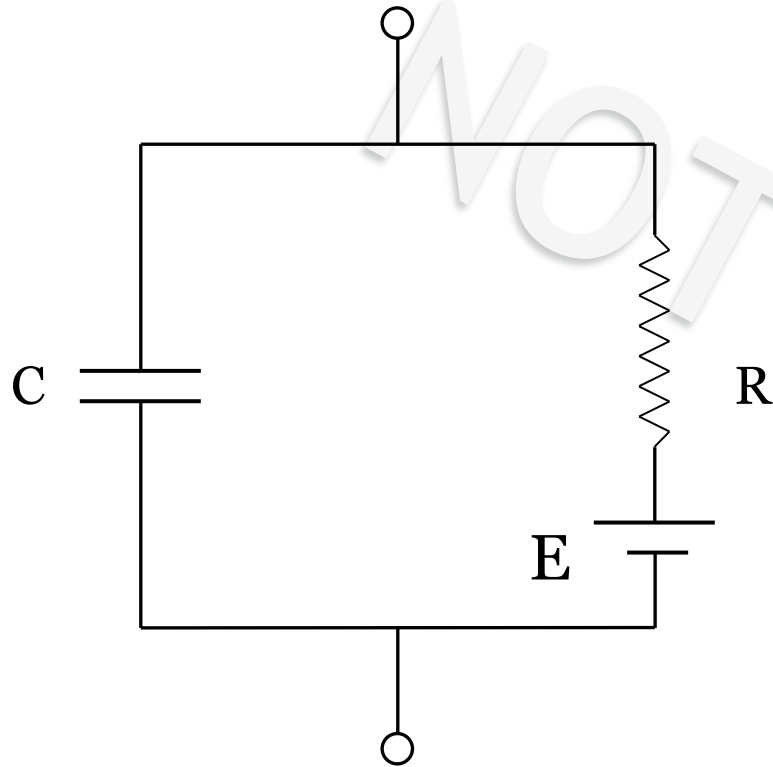


- Across a wire, the potential is the same
- The charge flowing into one element must equal the charge flowing out
- At a junction of wires, the total current is zero: Kirchhoff's law
- The potential changes by a fixed amount across a battery symbol
- The potential changes by a variable amount across a resistor symbol:
Ohm's law: $V = IR$ or $I = Vg$

Membrane patch

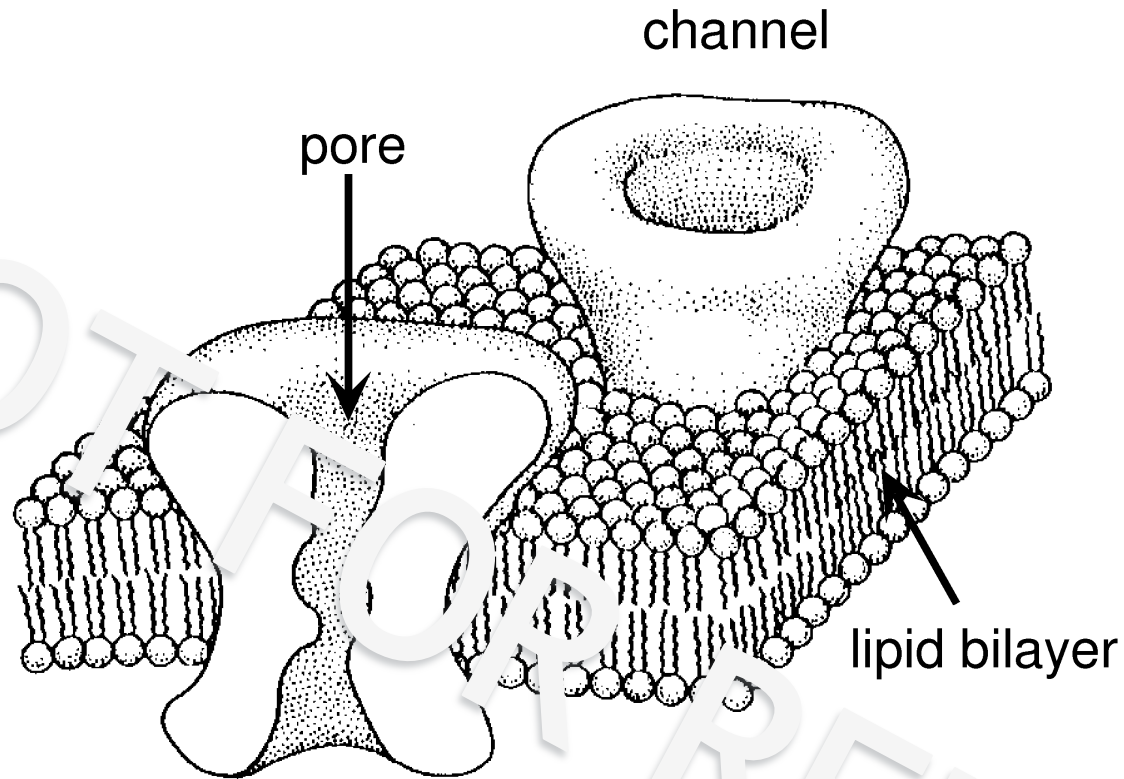

The passive membrane

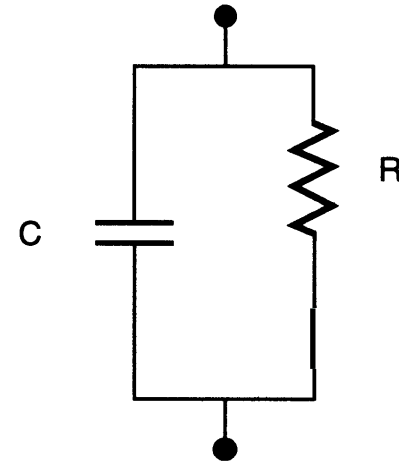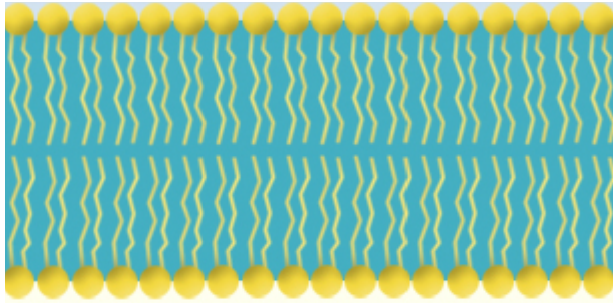



Kirchhoff: $I_R + I_C + I_{\text{ext}} = 0$

Ohm's law: $V = I_R R$


Capacitor: $C = Q/V$
 $I_C = C \frac{dV}{dt}$

$$C \frac{dV}{dt} = -\frac{V}{R} + I_{\text{ext}}$$

The cell has a battery

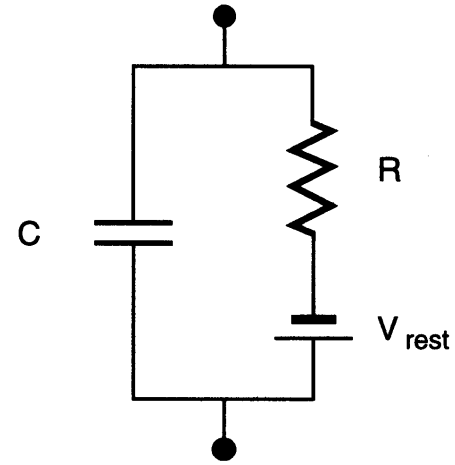
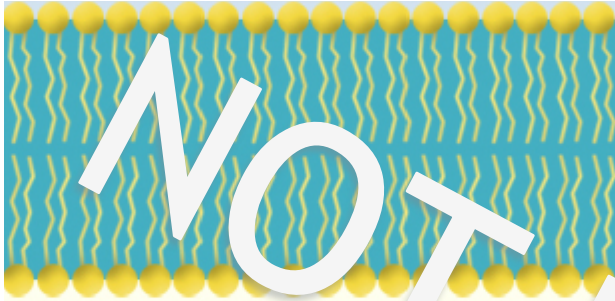


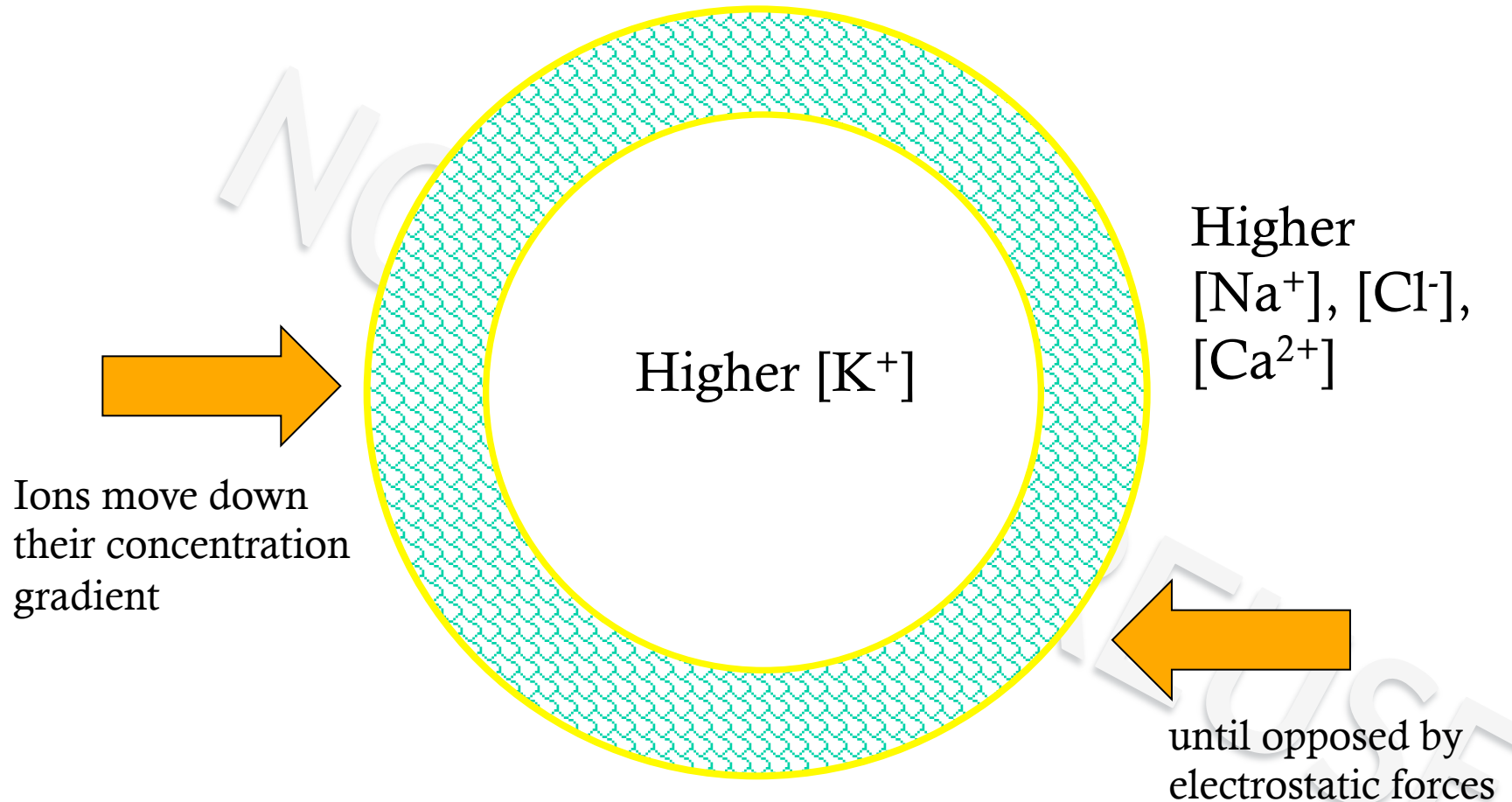The cell's battery: the equilibrium potential





Nernst:
$$E = \frac{k_B T}{zq} \ln \frac{[\text{inside}]}{[\text{outside}]}$$

The cell has a battery

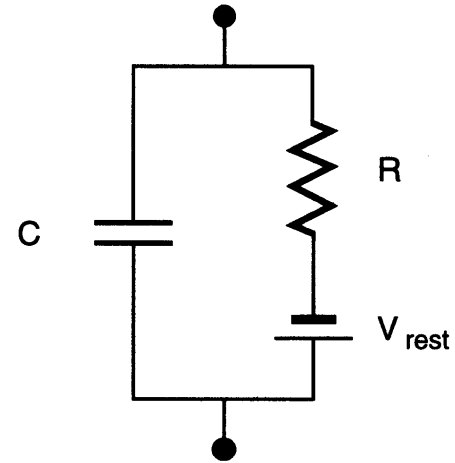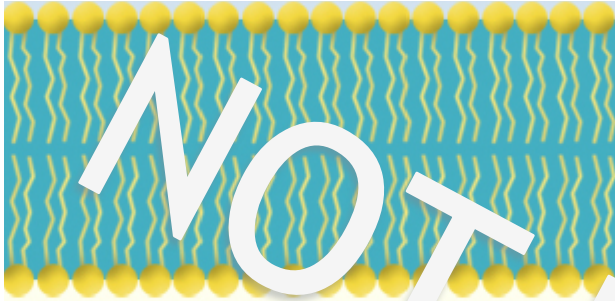

$$C \frac{dV}{dt} = -\frac{(V - V_{\text{rest}})}{R} + I_{\text{ext}}$$

How does such a membrane behave?

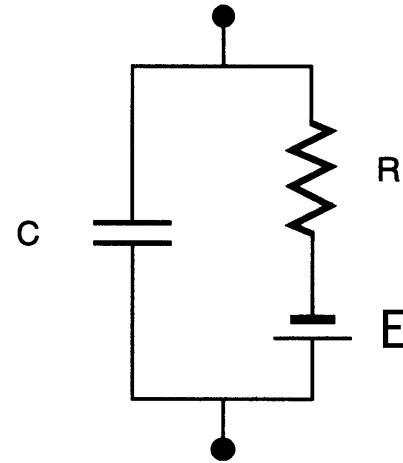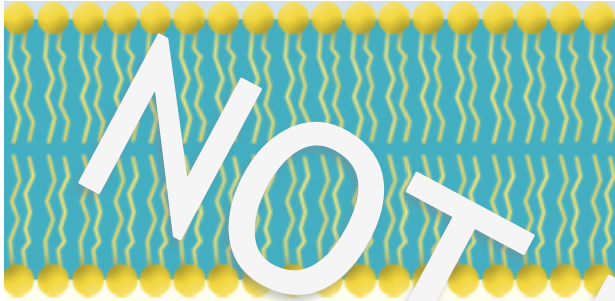

$$C_m = c_m A$$


$$c_m \approx 10 \text{ nF/mm}^2$$

$$R_m = r_m / A$$

$$r_m \approx 1 \text{ M}\Omega \text{ mm}^2$$

$$C \frac{dV}{dt} = -\frac{(V - V_{\text{rest}})}{R} + I_{\text{ext}}$$

$$\tau \frac{dV}{dt} = -V + V_{\infty}$$

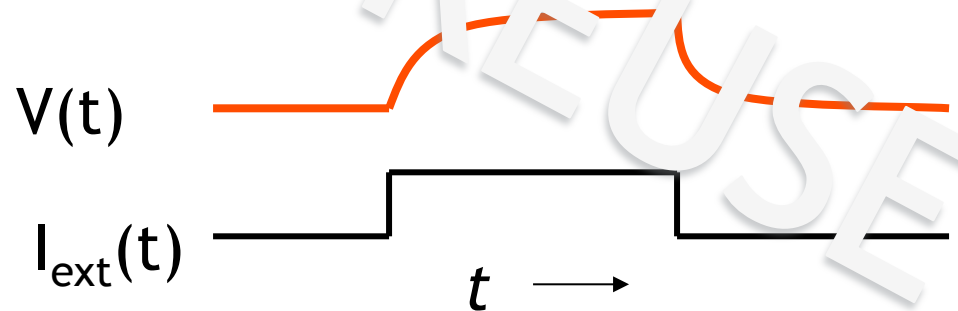


Each ion type is independent and has its own battery

Different ion channels have associated *conductances*.

A given conductance tends to move the membrane potential toward the equilibrium potential for that ion

E_{Na}	~	50mV	depolarizing
E_{Ca}	~	150mV	depolarizing
E_K	~	-80mV	hyperpolarizing
E_{Cl}	~	-60mV	shunting

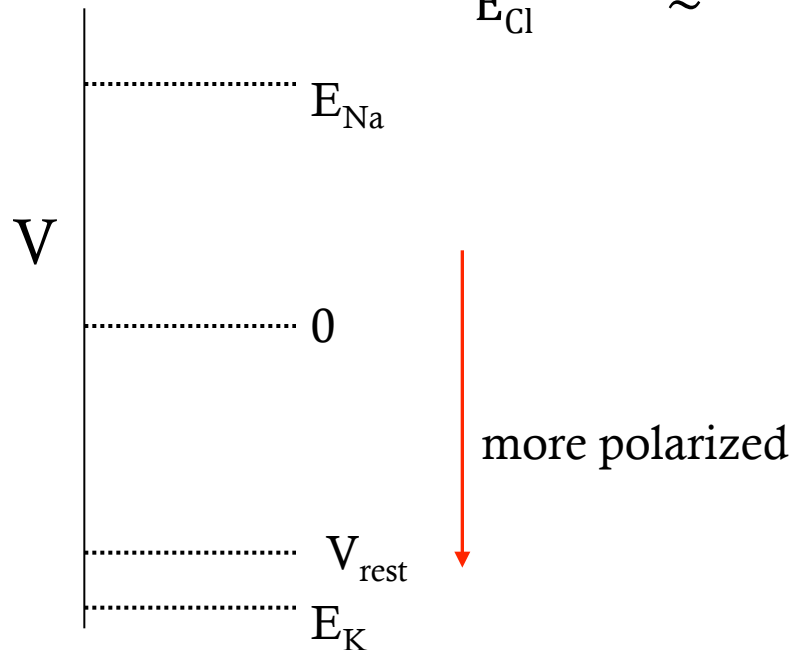

But what makes a neuron *compute*?

